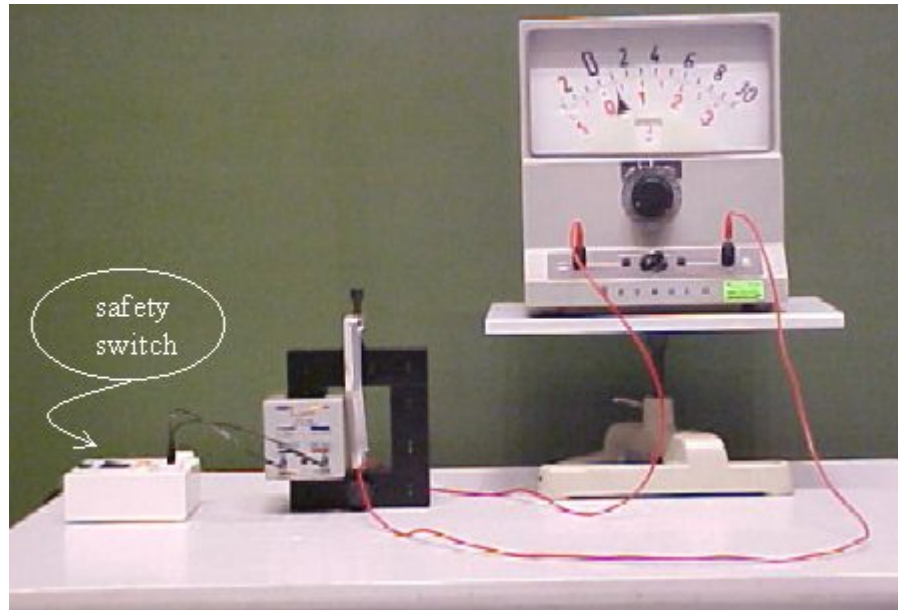


Transformer

Aim: To verify the relationship between the voltages and the number of turns in the coils.

Subjects: 5K30 (Transformers)

Diagram:



- Equipment:**
- 220V mains safety switchbox (we use Leybold 50206).
 - U-core with bar and clamping device.
 - Coil, $n=500$.
 - Multiscale voltmeter with large display.
 - Long wire.

- Safety:**
- Applying the 220V mains is done via a safety switchbox that switches both connectors ON/OFF. When ON, a red light appears on the box; when OFF a green light shows, indicating that it is safe to manipulate the circuit.

Transformer

Presentation: The demonstration is set up as shown in Diagram and Figure 1.

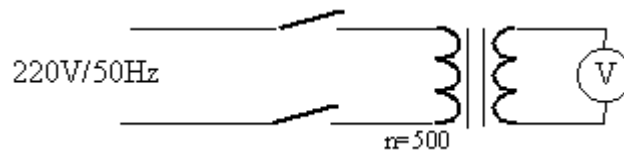


Figure 1

The 220V is switched on and the students can read on the V-meter that in the loop around the core a voltage of around .4V is induced. Then the demonstrator makes the wire go round the core in two loops. Again the induced voltage is read and a doubling is observed. Then make the wire go round the core three times (see Figure2). And so on, as long as the length of the wire enables it.

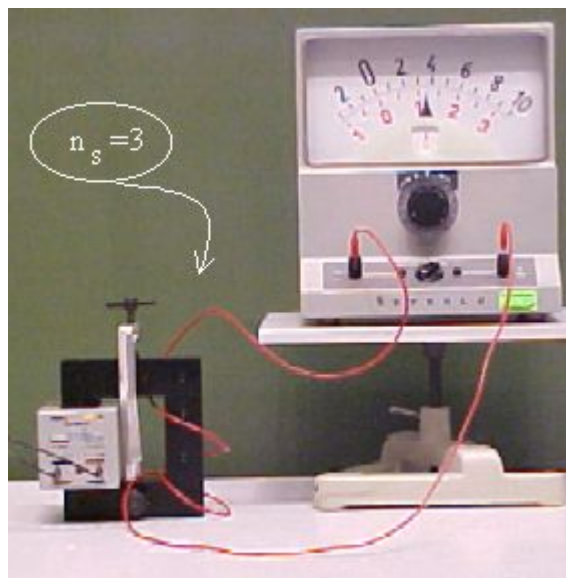


Figure 2

Clearly the proportionality between induced voltage and the number of turns is observed.

Explanation: When an alternating voltage (E_p) is applied across the primary coil of a transformer and there is no flux leakage, then the emf induced in the secondary coil is given by:

$$E_s = \frac{n_s}{n_p} E_p . \text{ This demonstration verifies this:}$$

- 1 turn: $E_s = 1/500(220) = .44V$.
- 2 turns: $E_s = 2/500(220) = .88V$.
- Etc.

Sources:

- [Mansfield, M and O'Sullivan, C., Understanding physics](#), pag. 527-529